

**Lab Session 4**  
**(19-23 Feb. 2024)**

**Objectives:**

On Simulink, perform the following activities:

[A] A single-phase power system consists of a 480-V 50-Hz generator supplying a load  $Z_{load} = 4 + j3 \Omega$  through a transmission line of impedance  $Z_{line} = 0.18 + j0.24 \Omega$ . Observe and report the following about this system.

- (1) Magnitude of line current and its phase angle.
- (2) Magnitude of load voltage and phase angle.
- (3) Phase difference between line current and the source voltage.
- (4) Phase difference between the load current and the load voltage.
- (5) Power loss in the transmission line.
- (6) Voltage drop across the line impedance.

[B] Suppose a 1:10 step-up transformer is placed at the generator end of the transmission line and a 10: 1 step-down transformer is placed at the load end of the line.

- (1) Magnitude of source, line and load current and respective phase angle.
- (2) Magnitude of load voltage and phase angle.
- (3) Phase difference between source current and the source voltage.
- (4) Phase difference between line current and the source voltage.
- (5) Phase difference between the load current and the load voltage.
- (6) Power loss in the transmission line.
- (7) Voltage drop across the line impedance.

[C] Report the observed difference of the power losses in the transmission line in the above two set-ups of the power system. Understand the importance of use of transformers in the power system.