

Sync. Gen.


$$I_F \rightarrow B$$

Related Quantities

(i) E_A with I_F (Mag. flux)


(ii) R_A & X_A

⇒ OPEN & SHORT CKT. TESTS

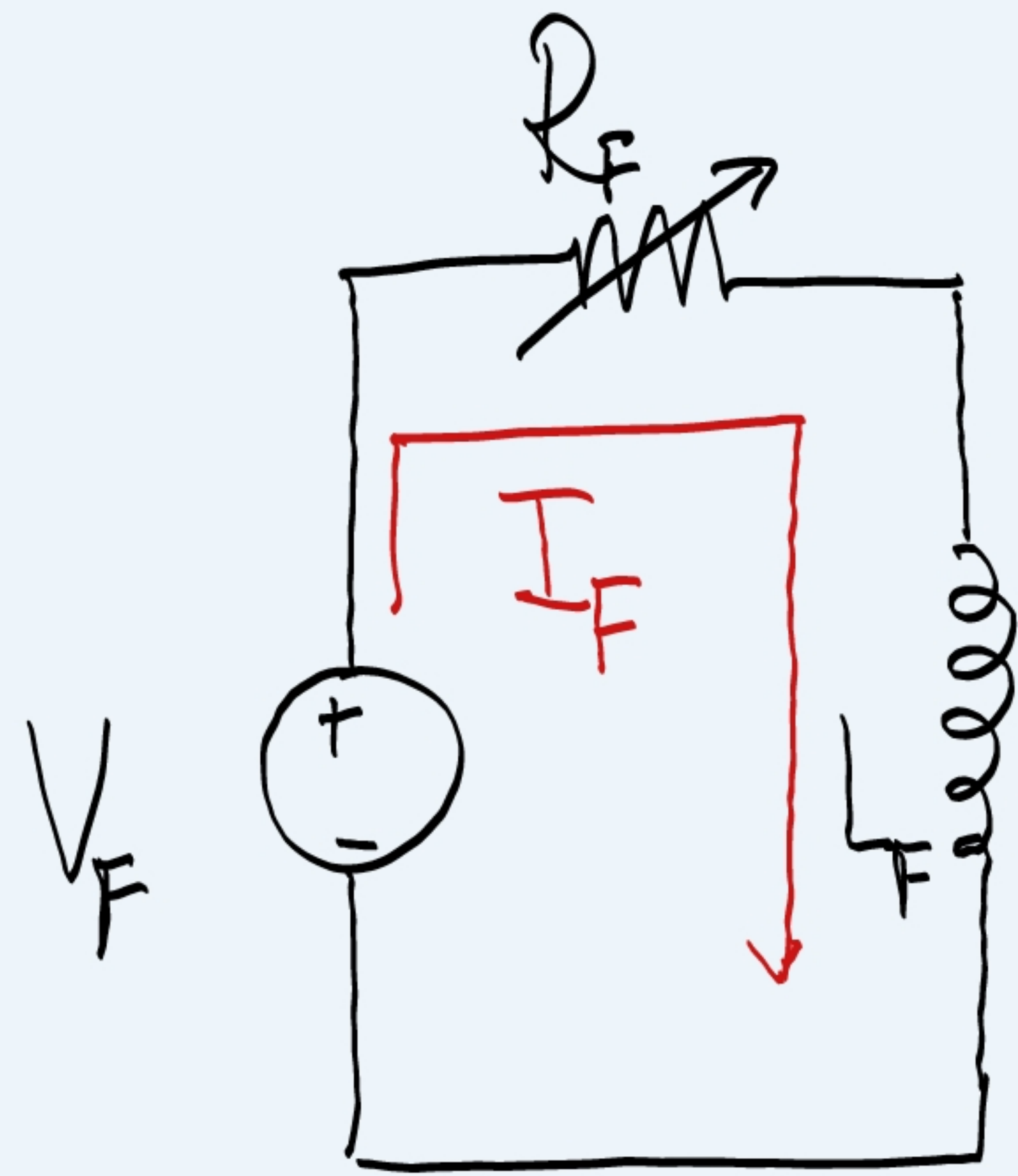

Rotor
(Connected with Prime Mover)

$$I_F = \frac{V_F}{R_F}$$

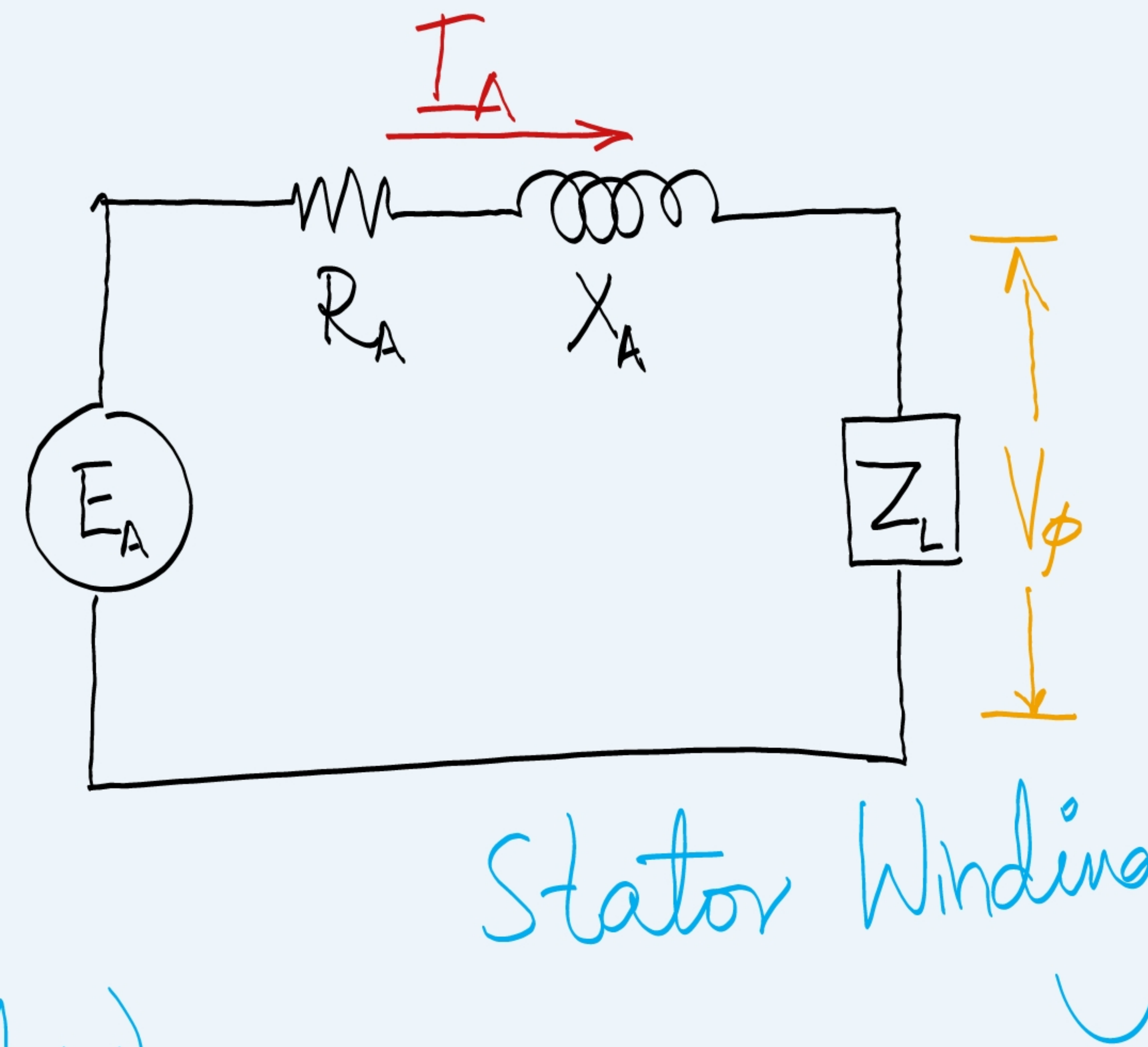


Stator Winding

$$E_A = I_A R_A + I_A X_A + V_\phi$$

$$E_A = \sqrt{2} \pi N_c \phi f$$

Open-Circuit test/characteristics (OCC):
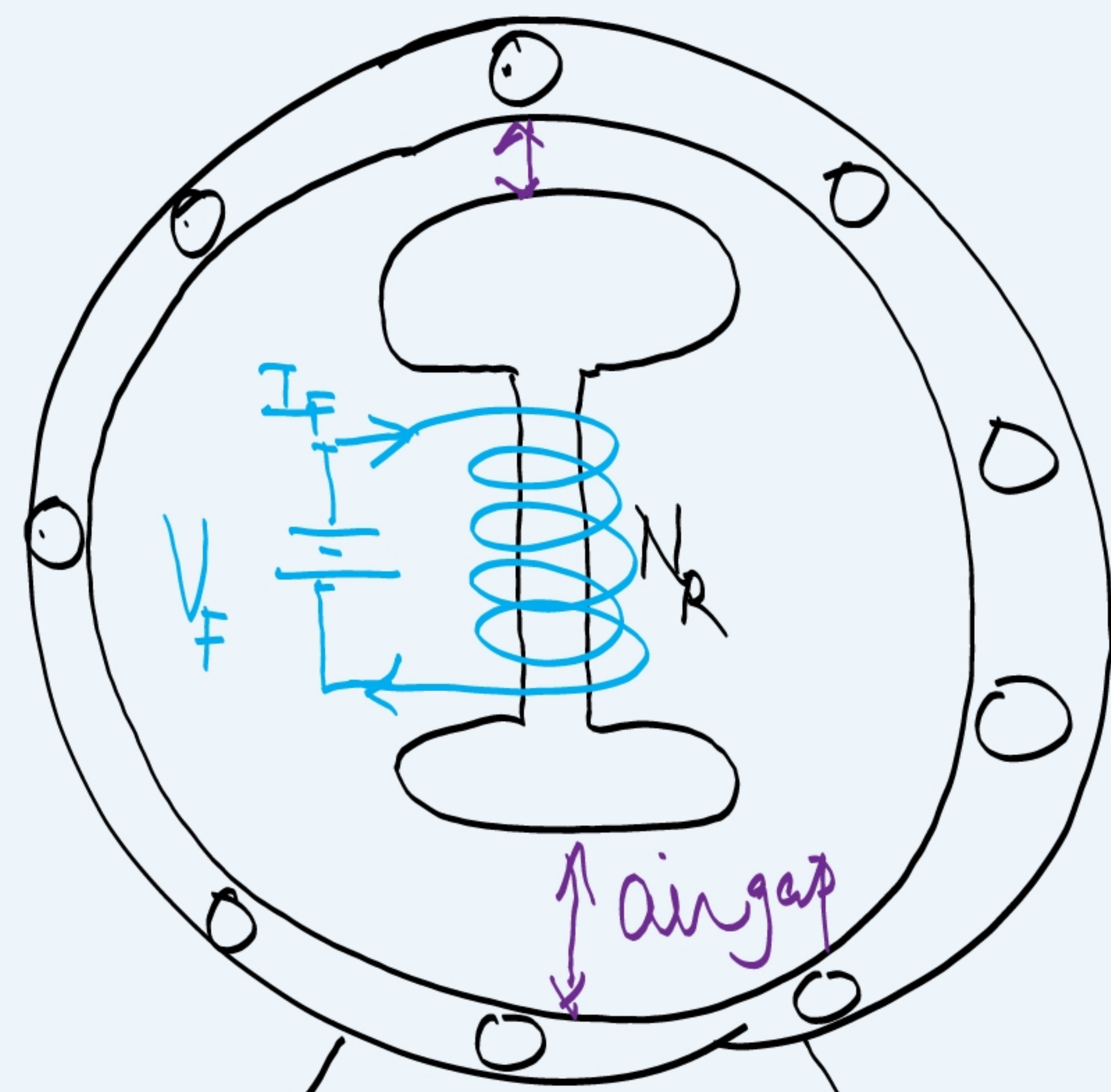
$$I_F N_R = \phi \mathcal{R}_{\text{Iron core}}$$



Load Z_L is not connected to stator winding

$$\Rightarrow I_A = 0$$

$$\Rightarrow V_\phi = E_A = V_{oc}$$



$$\mathcal{R} = \frac{l_c}{\mu A}; \quad \mathcal{R}_{\text{Iron}} = \frac{l_c}{\mu_0 \mu_{\text{iron}} A}; \quad \mathcal{R}_{\text{air gap}} = \frac{l_c}{\mu_0 A}$$


Short-ckt Test / Characteristics (SCC)

In armature winding, Remove Z_L and connect ammeter to measure I_A .

$$I_A = \frac{E_A}{\sqrt{R_A^2 + X_A^2}}$$

Assuming $X_A \gg R_A \Rightarrow I_A \sim \frac{E_A}{X_A}$

$$\Rightarrow X_A = \frac{E_A}{I_A}$$

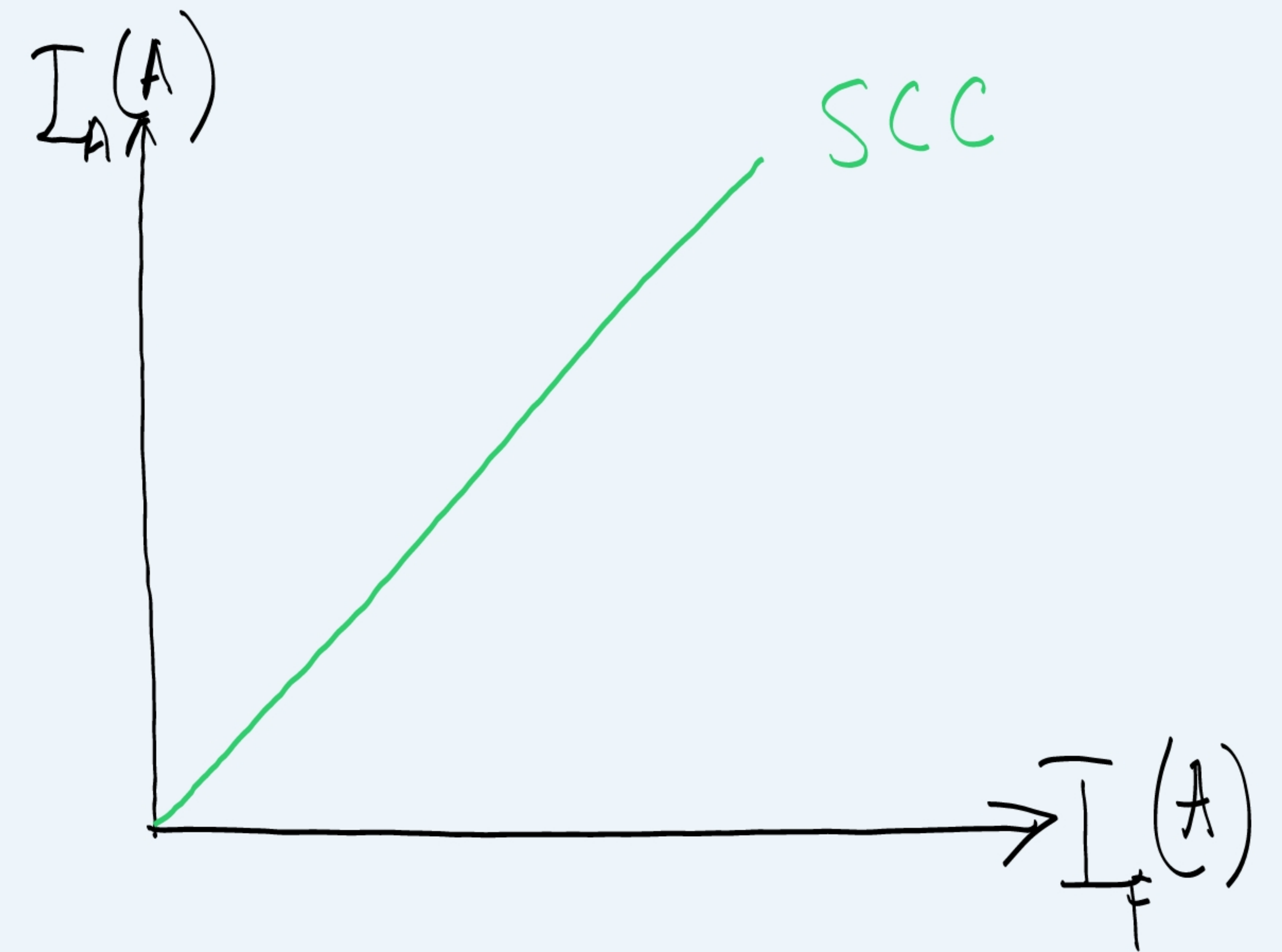


Problem 5.1

Sync. Gen.

1) Rated values: 200kVA, 480V, 50Hz, Y-connected

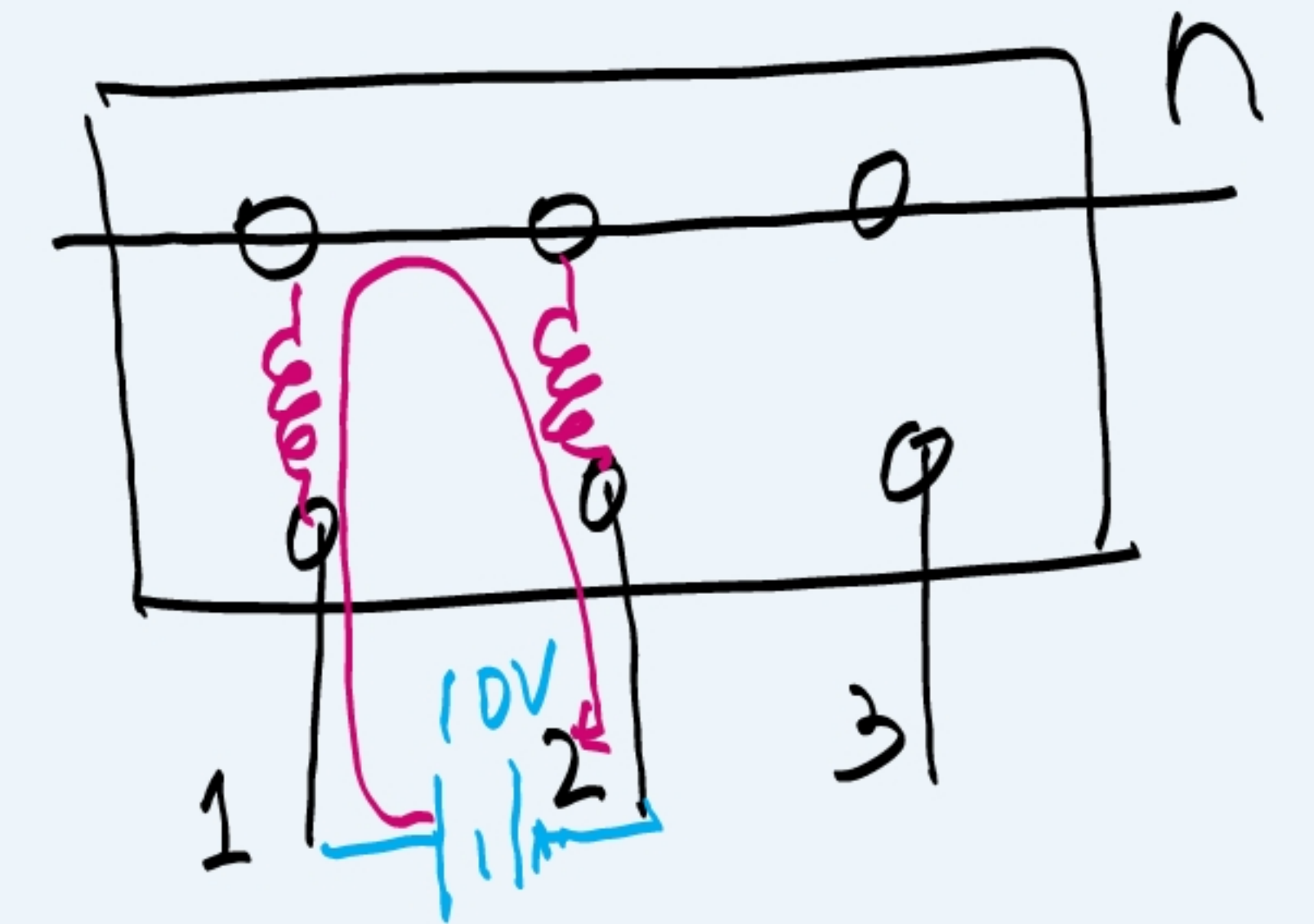2) Rated Field Current, $I_{F, \text{rated}} = 5 \text{ A}$



Test Results:

① $V_{T, \text{oc}}$ at $I_{F, \text{rated}} = 5 \text{ A}$ is 540V $\Rightarrow E_A = \frac{540\text{V}}{\sqrt{3}} = 312\text{V}$

② $I_{L, \text{sc}}$ at $I_{F, \text{rated}} = 5 \text{ A}$ is 300A $\Rightarrow I_A = 300 \text{ A}$

③ For $V_{\text{dc}} = 10 \text{ V}$; $I_A = 25 \text{ A} \Rightarrow 2R_A = \frac{10 \text{ V}}{25 \text{ A}} = 0.4 \Omega \Rightarrow R_A = 0.2 \Omega$

Assuming $X_s \gg 0.2 \Omega$

$$X_s = \frac{E_A}{I_A} = \frac{312V}{300A} = \underline{\hspace{2cm}}$$


$$\sqrt{R_A^2 + X_s^2} = \frac{E_A}{I_A} \Rightarrow X_s = \sqrt{\left(\frac{E_A}{I_A}\right)^2 - R_A^2} = \underline{\hspace{2cm}}$$

Problem 5.11 - 5.21

$$S = \sqrt{3} I_L V_L$$

Charac. Curves P5-2

Reference: 5.7

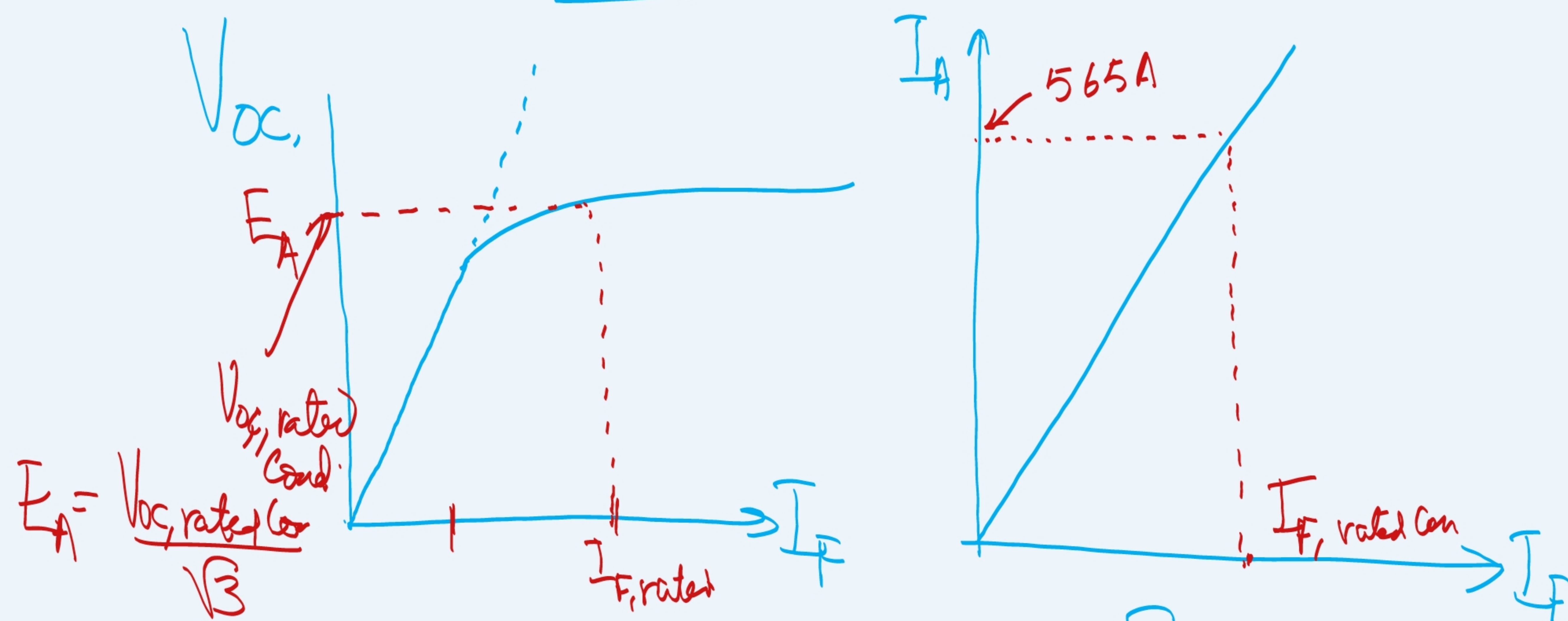

$$I_{A, \text{rated condition}} = I_L = \frac{S}{\sqrt{3} V_L} = \frac{470 \text{ kVA}}{\sqrt{3} \times 480 \text{ V}} = 565 \text{ A}$$

Sync. Gen.

- 1) Y-connected
- 2) Four poles
- 3) 470 kVA, 480 V, 60 Hz, 0.8 pf (lagging)
- 4) $R_A = 0.016 \Omega$
- 5) $P_{\text{loss}} = 7 + 8 \text{ kW} = 15 \text{ kW}$